

Combination Logic

January 5, 2018 12:21

Lab 1 Briefing

Purpose: re-acquainting with Quartus II design tools

Goal: Baccarat Game

Combination Blocks


- Based on combination logic (output is only dependant on the current inputs)
- Example such as adding
- No history
- Consists of Boolean gates but **not flip-flops** (which is used for memory)

The combination blocks that will be used are for:

1. 7 segment LED display
2. Computation of score of a hand

 Example of a basic combinational gate in Verilog:

```
1 module MY_SYSTEM(A, B, C);
2     ...input A, B;
3     ...output C;
4
5     ...assign C = A ^ B;
6 endmodule
7
```



Use **wire** to connect signals, consider this example:

```
1 module MY_SYS(A, B, C);
2     ...input A, B;
3     ...output C;
4     ...wire S0, S1;
5
6     ...assign S0 = A & ~B;
7     ...assign S1 = ~A & B;
8     ...assign C = S1 | S0;
9 endmodule
```

Recipe to create combinational components

1. Determine Boolean equation for each output
2. Write boolean equation as concurrent signal/wire assignments

Output change based on changes in the inputs

```
always @(<sensitivity list>)
begin
...<sequential statements>
end
```

A process is created this way and assignments of signals can be performed. Here's an example:

```
module MY_AND(A, B, C);
...input A, B;
...output C;
...reg C;

...always @(A or B)
...c = A & B;
endmodule
```

In this case, events of A and B should cause C to be re-evaluated. Since we are essentially "reading" A and B, they are in the *sensitivity list*

It is recommend to use **SystemVerilog**, so we use always_comb instead:

```
module MY_AND(A, B, C);  
    input A, B;  
    output C;  
    reg C;  
  
    always_comb  
        c = A & B;  
endmodule
```