

Introduction to Feedback

November 9, 2017 16:06


- Desensitize gain
- Reduce Distortion
- Extend BW
- Control I/O impedance
- ↑ Signal to noise ratio.

Recall OPamps has: $BW \sim 10\text{Hz}$
Gain $\sim 1 \times 10^6$

By having a gain of 100, BW would be 100kHz.

Voltage amplifier: High R_i , Low R_o
Current amplifier: Low R_i , High R_o .
Transconductance amplifier: Feedback drives up both R_i , R_o .
Transimpedance —: low R_i , R_o .

Basic Feedback Configuration

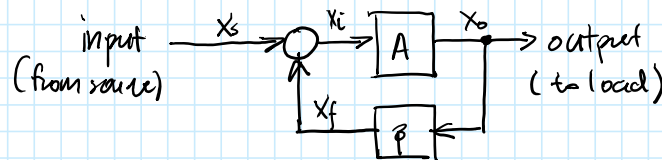

Ideally: $x_o = A x_i$

$x_f = \beta x_o$

$x_i = x_o - x_f$


$$A_f = \frac{x_o}{x_s} \quad A_f = \frac{A}{1 + A\beta}$$

If $A \gg \beta$, then $A_f \approx \frac{1}{\beta}$, so $x_f = \beta x_o = A\beta x_i = A\beta(x_s - x_f)$

$$\Rightarrow x_f = \frac{A\beta x_s}{1 + A\beta} \approx x_s \text{ for } A\beta \gg 1.$$

output follows the input.

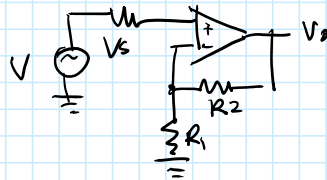Consider OPAMP with negative feedback (non-inverting)



\Rightarrow For $A \rightarrow \infty$, $V_p = V_s$ and $V_n = V_o \cdot \frac{R_1}{R_1 + R_2}$

Negative feedback: $V_n = V_p$

$$\text{So } A_f = \frac{V_o}{V_s} = \frac{\left(\frac{V_n (R_1 + R_2)}{R_2} \right)}{V_p} = \frac{R_1 + R_2}{R_1} = \frac{1}{\beta}$$

$$\therefore \beta = \frac{R_1}{R_1 + R_2}$$

\Rightarrow For $A = 10^4$ (gain), and $A_f = 100$ (gain of feedback)

→ For $A=10^4$ (gain), and $A_f=100$ (gain of feedback)

$$A_f = 100 = \frac{A}{1+A\beta} = \frac{10^4}{1 + \frac{10^4 R_1}{R_1+R_2}}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{10000}{99} - 1 = 100.01$$

→ If the open loop gain is only 7500, then:

$$A_f = \frac{7500}{1 + \frac{7500}{1+100.01}} \approx 99.67$$

We see that we changed base gain by 25% but the output gain didn't change that much.

→ Amount of feedback for $A_f=100$. ①

$$\begin{aligned} 1+A\beta &= 100 \\ &= 20 \log_{10} \left(1 + \frac{10^4}{1+100.01} \right) \\ &\approx 40 \text{ dB} \end{aligned}$$

Properties of Negative Feedback

Gain Desensitivity:

Recall that changing A by 25% → 0.33% change in A_f

$$\begin{aligned} \text{Thus } \frac{dA_f}{dA} &= \frac{1}{1+A\beta} - \frac{A\beta}{(1+A\beta)^2} \\ &= \frac{1}{(1+A\beta)^2} \end{aligned}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \frac{1}{1+A\beta}$$

$$\frac{dA_f}{A_f} = \frac{1}{1+A\beta} \frac{dA}{A}$$

$\boxed{1+A\beta}$: desensitivity factor.

Bandwidth Extension.

Consider open loop gain $A(s) = A_m \frac{\omega_H}{s + \omega_H}$ (Low pass, single pole)

$$= \frac{A_m}{\frac{s}{\omega_H} + 1}$$

$$\text{Then } A_f(s) = \frac{A(s)}{1+\beta A(s)} = \frac{A_m}{1 + \frac{s}{\omega_H} + A_m\beta}$$

$$A_{mf} = \frac{A_m}{1+A_m\beta}$$