 


Sequential Logic

January 8, 2018 12:13


Sequential Blocks

An example is a flip flop: The following is a 4-bit register



Positive D-Flip-Flop:
 
```
1 module DFF(D, CLK, Q);  
2   ...input D, CLK;  
3   ...output reg Q;  
4  
5   ...always @(posedge CLK)  
6   ...    Q <= D;  
7 endmodule
```



In SystemVerilog, the **always** keyword can be replaced with **always_ff**, which is safer.

Blocking vs. Non-blocking Assignments

Blocking

X = Y;

This will cause the assignment to happen immediately. So any succeeding assignments will use the new values

Non blocking

X <= Y;

This just says that X takes the value of Y at the end of the clock cycle. Thus any succeeding assignments will use the values at the beginning of the clock cycle. Thus ordering doesn't matter